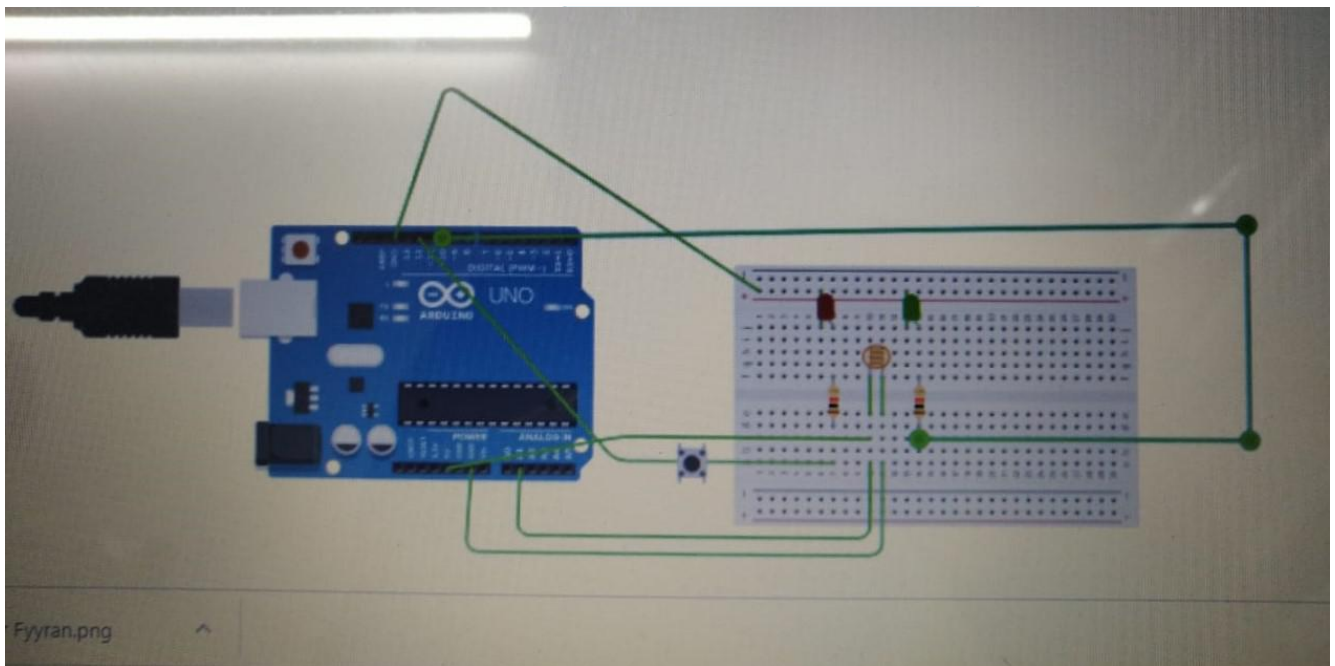


## REVALUATION

Ques. Design a DJ system that produces:

- Red light when a button is pressed during day.
- Green Light when a button is pressed during night.

CIRCUIT DIAGRAM:



### **Theory:**

Concepts used are:

- Working of LEDs (Light emitting diodes)
- Working of Arduino UNO
- Circuitry of Breadboard and it's use
- Code used to program the micro controller.

### **Arduino Uno circuit board:**

1. The arduino board can supply 5V as digital output signals from 14 pins (namely 0 to 13) present in it as digital input or output pins.
2. The GND pin of the arduino board acts as ground.

3. In our experiment we use digital pin 13 through which we connect positive terminal of LED and the negative terminal of LED is connected to the ground pin named as “gnd” on Arduino board.

4. Arduino is programmed to give output from digital pin 13 and gnd provide return pathway for current.

#### **Breadboard:**

In the circuit diagram of bread board present below, the two rows present at the top and bottom are connected with each other in series and the columns present in between are connected in a set of 5 are connected vertically.

#### **The Code used to program the micro-controller:**

In order to blink the led's we have to write a certain set of instruction in arduino IDE.

#### **Learning & Observations:**

- Coding in Arduino IDE is a very systematical way to show how the circuit is working.
- Arduino simplifies the process of working with microcontrollers
- Learnt the importance of calculated delay as the micro-controller is very fast and capable.
- Observed that there are many other interesting functions. Apart from void setup () and void loop () we can use our own function anywhere in the program.
  - How arduino can be used in our dialy life as the task given to us .

#### **Problems & Troubleshooting**

- We have to take at least 4 tries to find the right amount of delay so that one LED glows for the correct time interval .
- At first the LED was not working properly so we had to change and put a new LED in its place.

- *The circuit was not getting closed as the wires were not connected properly so I made sure that the connections were made properly.*
- *The required pattern was not getting created because of some error in the code so I had to change the code as per requirement.*
- *Proper closing of while using loops in the code.*
  - *Components were not available on tinkercad and the ones which were present we were not familiar with them .*
  - *Its difficult to stimulate on tinkercad because the task provided ar such which requires manual stimulation also.*

### ***Precautions***

- *Remember to declare all the ports used in digital input/output in correct way.*
- *Ensure that all wires are working correctly and all connections are tight.*
- *Remember to connect Negative end of device (in this case LED) to GND (ground) in Arduino Uno and positive end of each to a separate digital input output pin.*
- *Set right amount of delay so that circuit performs at its best.*

### ***Learning Outcomes:***

*From this experiment we learn and acquire skills about:*

- 1. How to make circuits using arduino board and bread board.*
- 2. Working of Arduino along with the LED.*
- 3. Application of digital pins of Arduino Uno Board.*